

# **A LAB MANUAL**

**on**

## **POWER SYSTEM ANALYSIS (20A02601P)**

**Prepared by**

**Dr.B.THRIVIKRAM**

**Assoc. Professor**

**Department of EEE**



**SREE RAMA ENGINEERING COLLEGE**

Approved by AICTE, New Delhi – Affiliated to JNTUA, Ananthapuramu

Accredited by NAAC with 'A' Grade

An ISO 9001:2015 & ISO 14001:2015 certified Institution

Rami Reddy Nagar, Karakambadi road, Tirupati-517507



# SREE RAMA ENGINEERING COLLEGE

Approved by AICTE, New Delhi – Affiliated to JNTUA, Ananthapuramu  
Accredited by NAAC with 'A' Grade  
Rami Reddy Nagar, Karakambadi road, Tirupati-517507



## Department of Electrical and Electronics Engineering

### POWER SYSTEMS ANALYSIS LAB

(20A02601P)

### III B.TECH II SEMESTER – EEE

#### List of Experiments

1. Determination of Sequence Impedances of Synchronous Machine
2. Determination of Sub-Transient Reactance of Salient Pole Synchronous Machine
3. L-G Fault Analysis on an Un Loaded Alternator
4. L-L Fault Analysis on Conventional Phases
5. Equivalent Circuit of a Three Winding Transformer
6. Y-Bus Formation Using Matlab
7. Z-Bus Formation Using Matlab
8. Gauss-Seidel Load Flow Analysis Using MATLAB
9. Newton Raphson Load Flow Analysis Using Soft Tools
10. Develop A Model for a Uncontrolled Single Area Load Frequency Control Problem and Simulate the Same Using Soft Tools

#### **Additional Experiments:**

1. Develop a Model for a Uncontrolled Two Area Load Frequency Control Problem and Simulate the Same Using Soft Tools.
2. Develop A Program to Solve Swing Equation by Point by Point Method Using Matlab

## INDEX

<b>S. No.</b>	<b>List of Experiments</b>	<b>Page No.</b>
1	Determination of Sequence Impedances of Synchronous Machine	2-4
2	Determination of Sub-Transient Reactance of Salient Pole Synchronous Machine	5-7
3	L-G Fault Analysis on an Un Loaded Alternator	8-9
4	L-L Fault Analysis on Conventional Phases	10-11
5	Equivalent Circuit of a Three Winding Transformer	12-17
6	Y-Bus Formation Using Matlab	18-19
7	Z-Bus Formation Using Matlab	20-22
8	Gauss-Seidel Load Flow Analysis Using MATLAB	23-25
9	Newton Raphson Load Flow Analysis Using Soft Tools	26-28
10	Develop A Model for A Uncontrolled Single Area Load Frequency Control Problem and Simulate the Same Using Soft Tools	29-30
11	Develop A Model for A Uncontrolled Two Area Load Frequency Control Problem and Simulate the Same Using Soft Tools.	31-33
12	Develop A Program to Solve Swing Equation by Point by Point Method Using Matlab	34-38

**DETERMINATION OF SEQUENCE IMPEDANCES OF SYNCHRONOUS MACHINE**


**Aim:** To determine the positive, negative and zero sequence impedances synchronous machine.

**Apparatus:**

S. No	Apparatus	Range	Quantity
1.	Alternator coupled to motor drive	415V, 1KVA, 1500RPM	1
2.	RPM meter	(1-9999) Digital	1
3.	Variac	1-Ø, 230/0-270V AC	1
4.	Patch chords	-	As per requirement


**Circuit Diagrams:**

- 1 To determine positive sequence impedance of synchronous machine

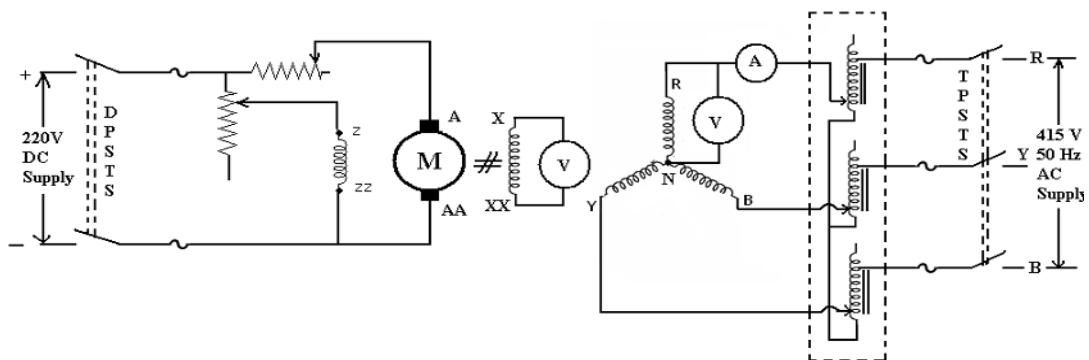


**Fig-1.1 positive sequence impedance of synchronous machine**

- 2 To determine negative sequence impedance of synchronous machine

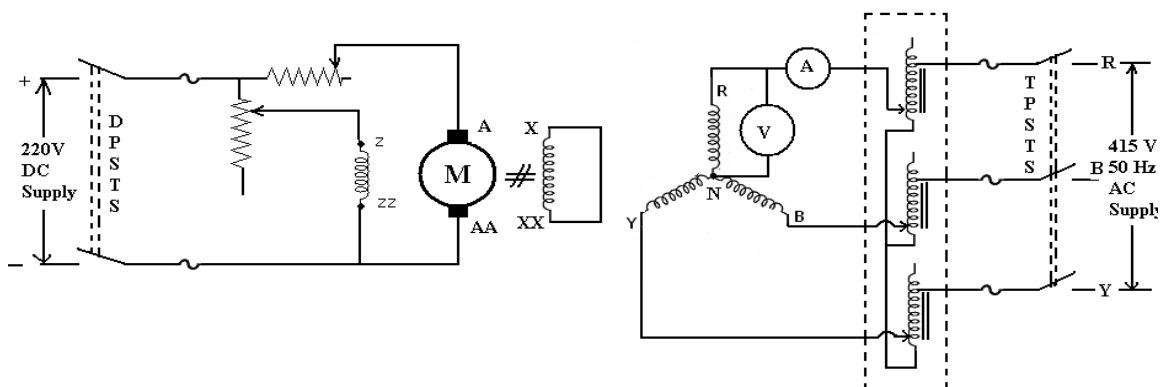

**Fig-1.2 positive sequence impedance of synchronous machine**

- To determine zero sequence impedance of synchronous machine

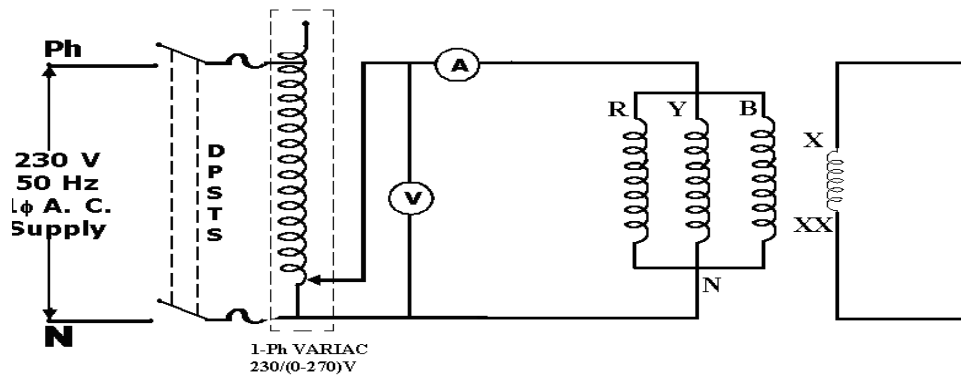

**Fig- 1.3 Zero Sequence Impedance of Synchronous Machine**

**Procedure:**

**Positive Sequence:**

- Connections are made as per the circuit diagram 1
- Observing the precautions close the DPST switch
- Vary the armature and field rheostats of DC motor such that the synchronous machine runs at rated speed.
- Close the TPST switch and vary three phase auto transformer in steps of 5 volts ranging from 50V – 70V are injected into the stator and note down all the meter readings in each step.
- The positive sequence reactance is calculated by the formula  $Z_1 = V_1 / I_1$

**Negative Sequence:**

- Connections are made as per the circuit diagram 2
- Observing the precautions close the DPST switch
- Vary the armature and field rheostats of DC motor such that the synchronous machine runs at rated speed.
- Close the TPST switch and vary three phase auto transformer in steps of 5 volts up to 70V are injected into the stator and note down all the meter readings in each step.
- The negative sequence reactance is calculated by the formula  $Z_2 = V_2 / I_2$

**Zero Sequence:**

- Connections are made as per the circuit diagram 3.
- Observing the precautions close the DPST switch.
- Vary the single phase auto transformer in steps up to rated current of the machine and note down all the meter readings in each step.
- The zero sequence reactance is calculated by the formula  $Z_0 = V_0 / (\sqrt{3}I_0)$

**Tabular column to find positive, negative and zero sequence impedances:**

S.No.	Positive Sequence			Negative Sequence			zero sequence		
	V <sub>1</sub> (V)	I <sub>1</sub> (A)	Z <sub>1</sub> Ω	V <sub>2</sub> (V)	I <sub>2</sub> (A)	Z <sub>2</sub> Ω	V <sub>0</sub> (V)	I <sub>0</sub> (A)	Z <sub>0</sub> Ω

**Model Calculations:**

$$Z_1 = V_1 / I_1$$

$$Z_2 = V_2 / I_2$$

$$Z_0 = V_0 / (\sqrt{3}I_0)$$

**Precautions:**

1. Avoid loose connections
2. Readings should be taken without parallax error
3. Auto transformer should be in minimum voltage position.

**Result:**


**DETERMINATION OF SUB-TRANSIENT REACTANCE OF SALIENT POLE SYNCHRONOUS MACHINE**

**Aim:** To determine sub-transient direct axis reactance and sub transient quadrature axis reactance of salient pole synchronous machine.

**Apparatus:**

S. No	Apparatus	Range	Quantity
1.	Alternator coupled to motor drive	415V, 1KVA, 1500RPM	1
2.	RPM meter	(1-9999) Digital	1
3.	Variac	1-Ø, 230/0-270V AC	1
4.	Ammeter	0-2A MI	1
5.	Ammeter	0-2A MC	1
6.	Voltmeter	0-150V MI	1
7.	Patch chords	-	As per requirement

**Circuit Diagram:**

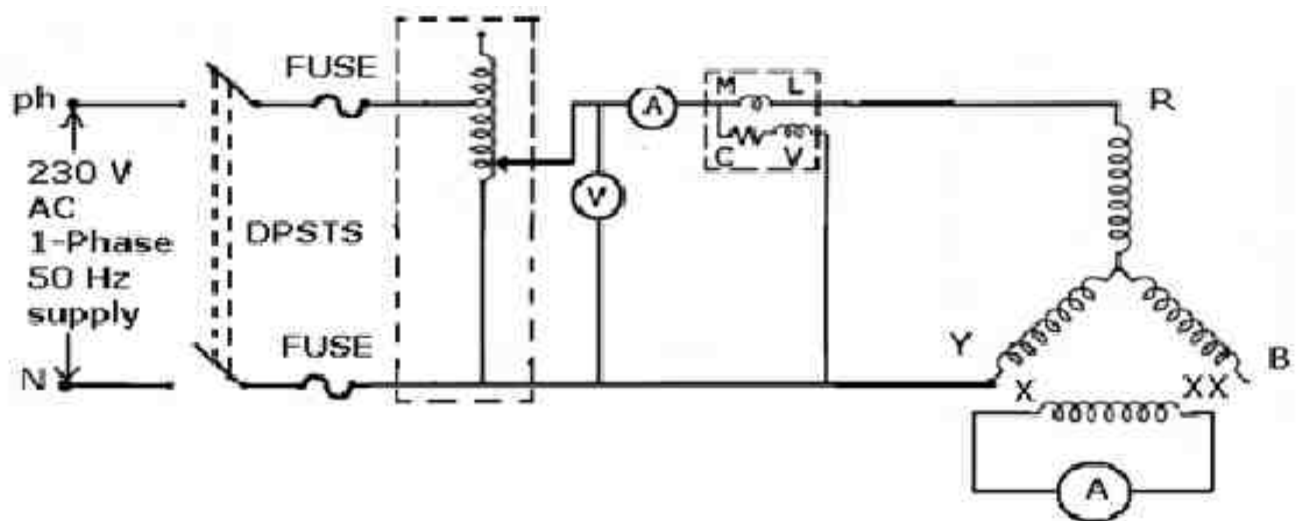

**Fig- 2.1: Sub-Transient Reactance of Salient Pole Synchronous Machine**

**Procedure:**

1. Connections are made as per the circuit diagram
2. By varying variac apply some voltage across the stator of alternator. (60, 70, 100V)
3. Twist the mechanical coupling, so that we get maximum and minimum armature currents.
4. Tabulate the readings.
5. Repeat the procedure for other three or four readings.
6. Calculate  $X_d''$  &  $X_q''$ .

**Tabular column for minimum field current:**

S.No.	I <sub>qmin</sub> (A)	V <sub>qmin</sub> (V)	W <sub>qmin</sub>		Cosθ <sub>q</sub>	Z <sub>q</sub> '' Ω/ph	X <sub>q</sub> '' Ω/ph
			Meas	Act			

**Tabular column for maximum field current:**

S.No.	I <sub>qmax</sub> (A)	V <sub>qmax</sub> (A)	W <sub>qmax</sub>		Cosθ <sub>d</sub>	Z <sub>q</sub> '' Ω/ph	X <sub>q</sub> '' Ω/ph
			Meas	Act			

**Model calculations:**

For minimum value of field current at V<sub>q</sub> min

$$\text{Cos}\theta_q = \frac{W_{d \min} / 2}{V_{q \min} / 2 * I_{q \min}}$$

$$Z_q'' = \frac{V_{q \min} / 2}{I_{q \min}}$$

$$X_q'' = Z_q'' \sin\theta_q$$

For Maximum value of field current at V<sub>d</sub> max

$$\text{Cos}\theta_d = \frac{W_{d \max} / 2}{V_{q \max} / 2 * I_{d \max}}$$

$$Z_q'' = \frac{V_{q \max} / 2}{I_{d \max}}$$

$$X_d'' = Z_d'' \sin\theta_d$$



**Precautions:**

1. Avoid loose connections
2. Readings should be taken without parallax error
3. Auto transformer should be in minimum position.

**Result:**

**L-G FAULT ANALYSIS ON AN UN LOADED ALTERNATOR**


**AIM:** To determine the fault current on an alternator under LG fault conditions

**Apparatus Required:**

S.No	Name of the apparatus	Range	Quantity
1	Alternator coupled to motor drive	415V, 1KVA, 1500RPM	1
2	RPM meter	(1-9999) Digital	1
3	Variac	1- $\emptyset$ , 230/0-270V AC	1
4	Ammeter	(0-2A) MI	1
5	Voltmeter	(0-600V) MI	1
6	Patch chords	-	As per requirement

**L-G Fault:**

**Circuit Diagram:**

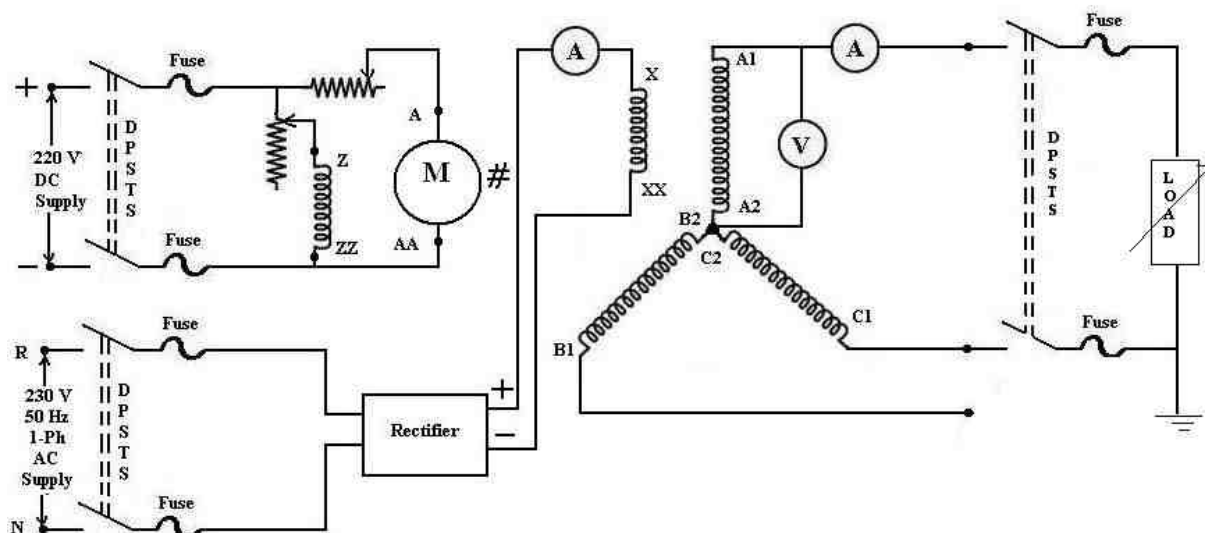

**Fig - 3.1: L-G Fault Analysis on An Un Loaded Alternator**

**Procedure:**

1. Connect the circuit as per the circuit diagram of L-G fault
2. Observing the precautions, close the DPST<sub>1</sub> switch
3. Field rheostat of motor is adjusted such that the rated speed of the synchronous machine is obtained.
4. Close the DPST<sub>2</sub> switch and apply 230V by varying the rectifier and load is applied in steps up to rated current and note down the corresponding current & voltage readings.
5. Tabulate current and voltage readings.

**Tabular Column to find L-G Fault Current:**

S.no	Current I	Voltage V	Fault Impedance Z <sub>f</sub>	Fault current I <sub>f</sub>
	(Amps)	(Volts)	(Ohms)	(Amps)

**Model Calculations:**

**L-G Fault:**

Fault current =  $3I_a^0$ ,  $I_a = \frac{3Ea}{Z_1 + Z_2 + Z_0 + 3Z_f}$

Fault impedance  $Z_f = \frac{V}{I}$

Fault current =

**Precautions:**

1. Avoid loose connections and wrong connections.
2. Keep the field Rheostat of motor in minimum resistance position and armature rheostat of motor in maximum resistance position.
3. DPST switch must be kept open initially.
4. Initially rectifier must be in minimum position.

**Result:**

L-L FAULT ANALYSIS ON CONVENTIONAL PHASES

AIM: To determine the fault current on an alternator under L-L fault conditions

Apparatus Required:

S.No	Name of the apparatus	Range	Quantity
1	Alternator coupled to motor drive	415V, 1KVA, 1500RPM	1
2	RPM meter	(1-9999) Digital	1
3	Variac	1- $\emptyset$ , 230/0-270V AC	1
4	Ammeter	(0-2A) MI	1
5	Voltmeter	(0-600V) MI	1
6	Patch chords	-	As per requirement

Circuit Diagram:

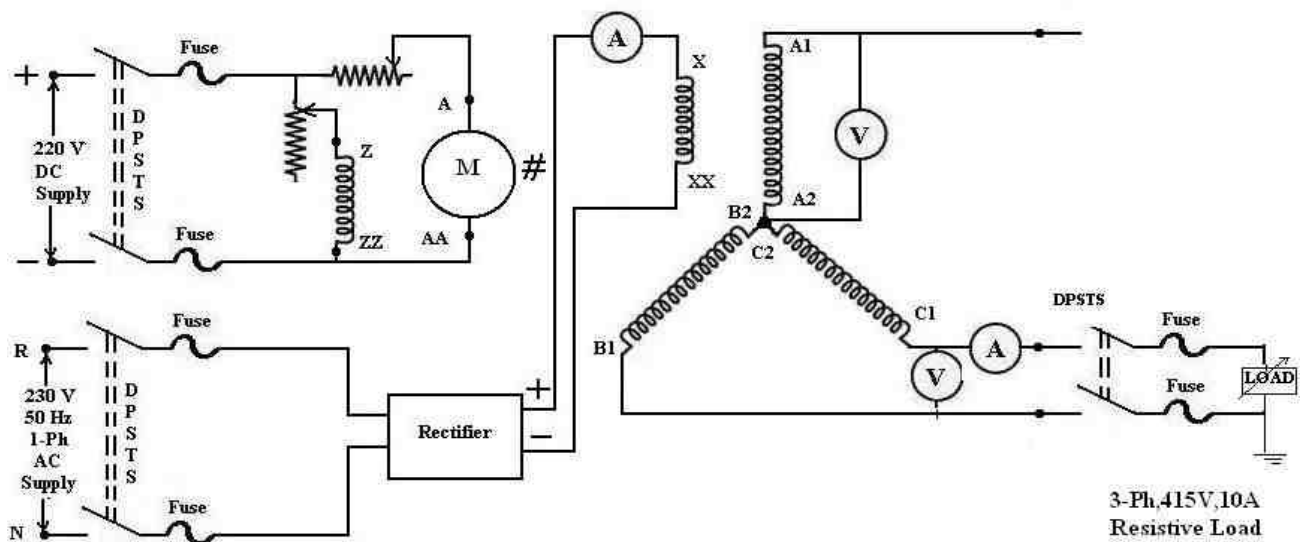


Fig- 4.1: L-L Fault

Procedure:

1. Connect the circuit as per the circuit diagram of L-L fault.
2. Observe the precautions, close the DPST<sub>1</sub> switch.
3. Adjust the field rheostat of dc motor such that the rated speed of the synchronous machine is obtained.
4. Close the DPST<sub>1</sub> switch and apply the field voltage 415V by varying the rectifier.
5. Close the DPST<sub>2</sub> switch and 3- Ph load is varied in steps up to rated current.
6. Tabulate current and voltage readings.

**Tabular Column to find L-L Fault Current:**

S.no	Current I	Voltage V	Fault Impedance $Z_f$	Fault current $I_f$ or $I_b$
	(Amps)	(Volts)	(Ohms)	(Amps)

**Model Calculations:**

**L-L Fault:** Fault impedance  $Z_f = \frac{V}{I}$

$$I_a = \frac{E_a}{Z_1 + Z_2 + Z_f} =$$

$$I_f = \sqrt{3} I_a =$$

**Precautions:**

1. Avoid loose connections and wrong connections.
2. Keep the field Rheostat of motor in minimum resistance position and armature rheostat of motor in maximum resistance position.
3. DPST switch must be kept open initially.
4. Initially rectifier must be in minimum position.

**Result:**

**EQUIVALENT CIRCUIT OF A THREE WINDING TRANSFORMER**

**Aim:** To draw the Equivalent Circuit of a Three Winding Transformer by conducting Open circuit and Short Circuit Tests.

**Apparatus:**


- Three Winding Transformer Trainer Set up
- Patch Cards

**Name Plate Details:**

- Capacity 1 KVA
- Primary 0-230VAC
- Secondary-1 0-110VAC
- Secondary-2 0-64VAC

**Circuit Diagram:**

**For Open Circuit Test** (Primary excited & both secondary's are open)

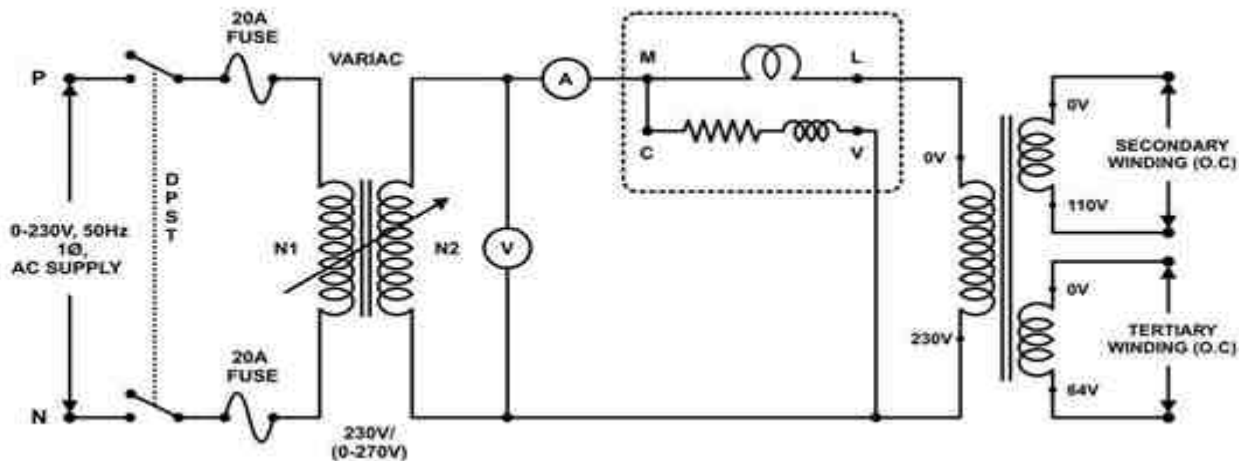

**Fig- 5.1: Three Winding Transformer**

**Procedure:**

1. Connections are made as per the above Diagram-1, Connect digital Ammeter, Voltmeter & Power meter as per diagram
2. Keep the dimmer stat in zero (minimum) position.
3. Switch ON the main MCB.
4. Slowly apply the rated input voltage i.e., 220V to the primary of the transformer by varying the dimmer stat.
5. Note down the readings of Voltmeter, Ammeter and Wattmeter.

**Tabular Column:**

Voltage (V)	Current (A)	Power (W)


**Theoretical Calculations:**

Power factor,  $\cos\phi_0 = W_0 / V_0 * I_0$

Core loss resistance,  $R_0 = V_0 / I_0 * \cos\phi_0$

Magnetizing Reactance,  $X_0 = V_0 / I_0 * \sin\phi_0$

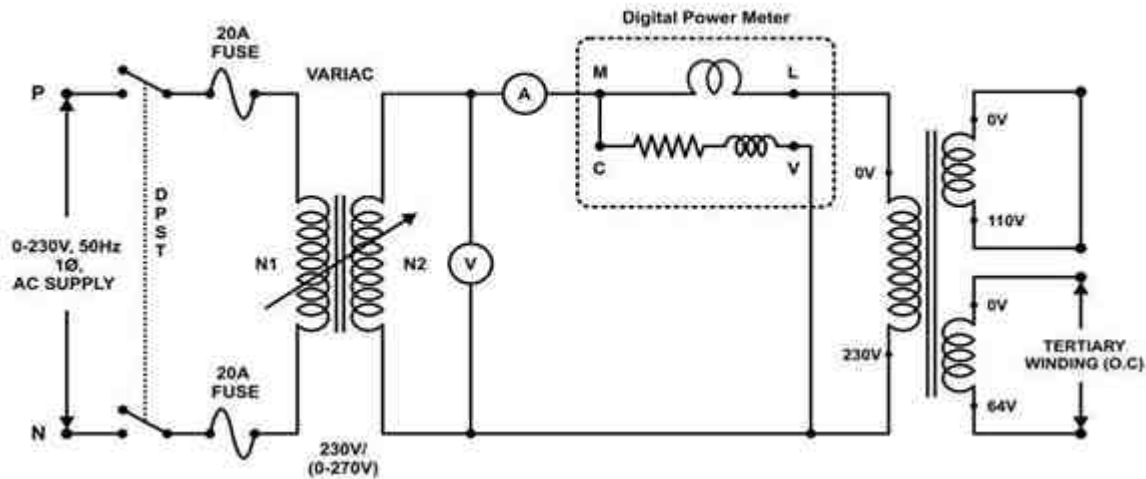**For Short Circuit Test-1** (Primary excited & Secondary Shorted & tertiary winding Open)



**Procedure:**

1. Connections are made as per the above connection diagram
2. Short Circuit the Secondary winding of the transformer .
3. Keep the dimmer stat in zero (minimum) position.
4. Switch ON the main MCB.
5. Gradually increase the voltage up to the transformer rated current (5A) by varying the dimmer stat.
6. Note down the readings of Voltmeter, Ammeter and Wattmeter.

**Tabular Column:**


Voltage (V)	Current (A)	Power (W)

**Theoretical Calculations:**

$$Z_{12} = V_1 / I_1 =$$

$$r_{12} = P_1 / I_1^2 =$$

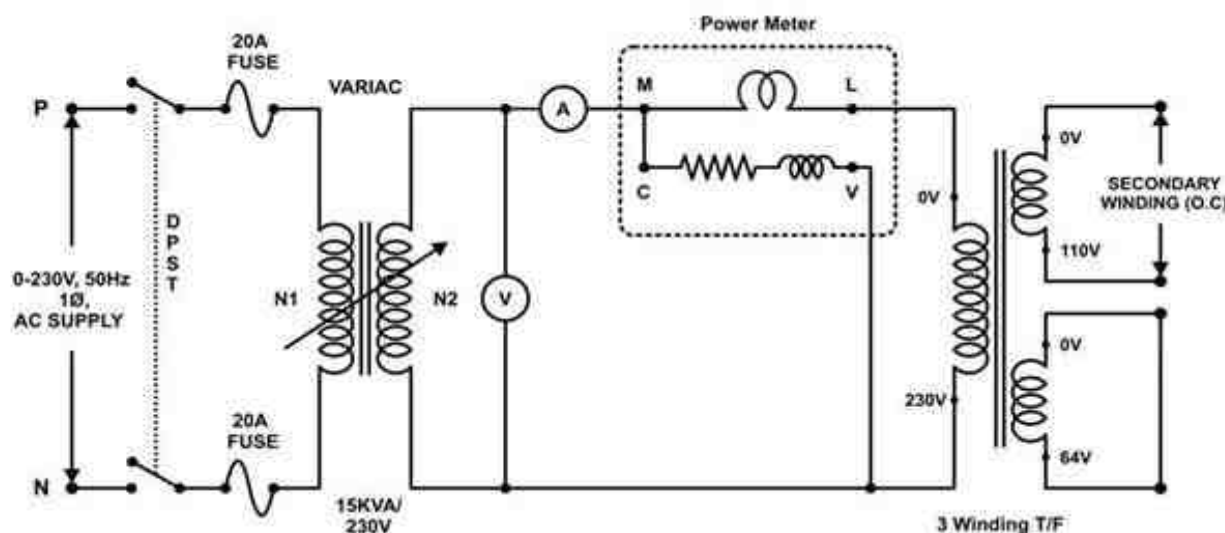**Short Circuit Test-2** (Primary excited & Secondary (110V) open & tertiary winding (64V) Shorted



**Procedure:**

1. Connections are made as per the above connection diagram
2. Short Circuit the Secondary winding (64v) of the transformer .
3. Keep the dimmer stat in zero (minimum) position.
4. Switch ON the main MCB.
5. Gradually increase the voltage up to the transformer rated current (5A) by varying the dimmer stat.
6. Note down the readings of Voltmeter, Ammeter and Wattmeter

**Tabular Column:**

Voltage (V)	Current (A)	Power (W)


**Theoretical Calculations:**

$$Z_{13} = V_2 / I_2 =$$

$$r_{13} = P_2 / I_2^2 =$$

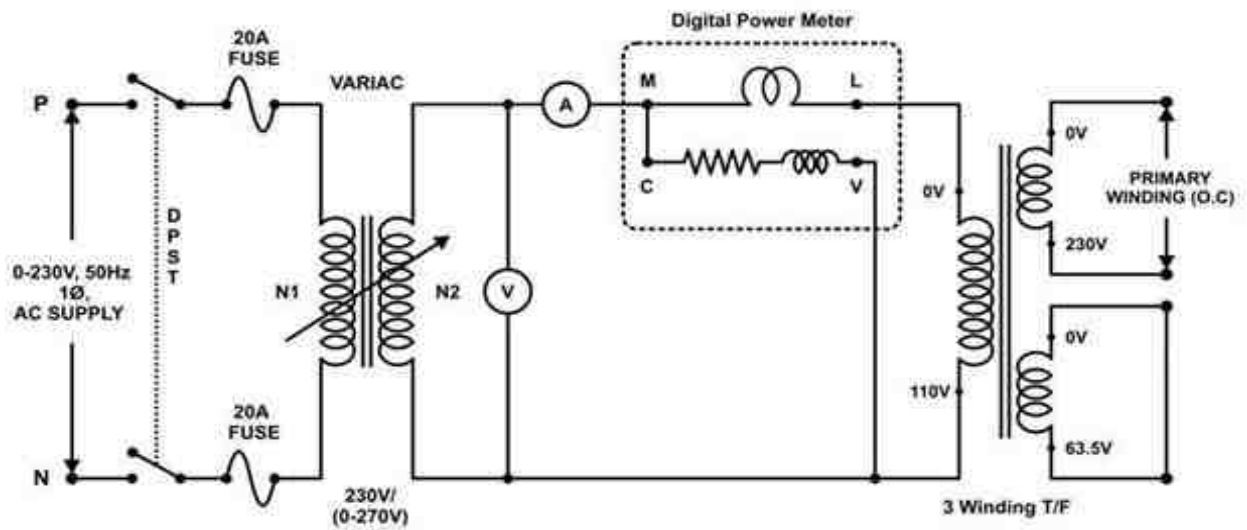**Short Circuit Test-3** (Secondary (110v) excited & Primary open & tertiary winding (64V) Shorted





**Procedure:**

1. Connections are made as per the above connection diagram
2. Short Circuit the Secondary winding (64v) of the transformer .
3. Keep the dimmer stat in zero (minimum) position.
4. Switch ON the main MCB.
5. Gradually increase the voltage up to the transformer rated current (5A) by varying the dimmer stat. ( note do not apply more than 110VAC)
6. Note down the readings of Voltmeter, Ammeter and Wattmeter

**Tabular Column:**

Voltage (V)	Current (A)	Power (W)

**Theoretical Calculations:**

$$Z_{23} = V_3 / I_3 =$$

$$R_{23} = P_3 / I_3^2 =$$

Transferring both values to primary side

$$Z_{23}^1 = Z_{23} \times \left(\frac{N_1}{N_2}\right)^2 =$$

$$\gamma_{23}^1 = \gamma_{23} \times \left(\frac{N_1}{N_2}\right)^2 =$$

The equivalent circuit resistance  $r_1, r_2, r_3$  are

$$r_1 = \frac{1}{2} (r_{12} + r_{13} - r_{23}^1)$$

$$=$$

$$r_2 = \frac{1}{2} (r_{12} + r_{23}^1 - r_{13})$$

$$=$$

$$r_3 = \frac{1}{2} (r_{23}^1 + r_{13} - r_{12})$$

Leakage impedance referred to primary side,

$$Z_1 = \frac{1}{2} (Z_{12} + Z_{13} - Z_{23}^1)$$

$$=$$

$$Z_2 = \frac{1}{2} (Z_{12} + Z_{23}^1 - Z_{13})$$

$$=$$

$$Z_3 = \frac{1}{2} (Z_{13} + Z_{23}^1 - Z_{12})$$

Leakage Reactances referred to primary side,

$$X_1 = \sqrt{Z_1^2 - r_1^2}$$

$$=$$

$$X_2 = \sqrt{Z_2^2 - r_2^2}$$

$$=$$

$$X_3 = \sqrt{Z_3^2 - r_3^2}$$

Leakage impedance referred to primary winding,

$$X_1 = r_1 + j X_1 =$$


Leakage impedance of secondary winding referred to primary side,

$$Z_2 = r_2 + j X_2 \left(\frac{N_2}{N_1}\right)^2$$

Leakage impedance of tertiary winding referred to primary side,

$$Z_3 = r_3 + j x_3 \left( \frac{N_2}{N_1} \right)^2$$

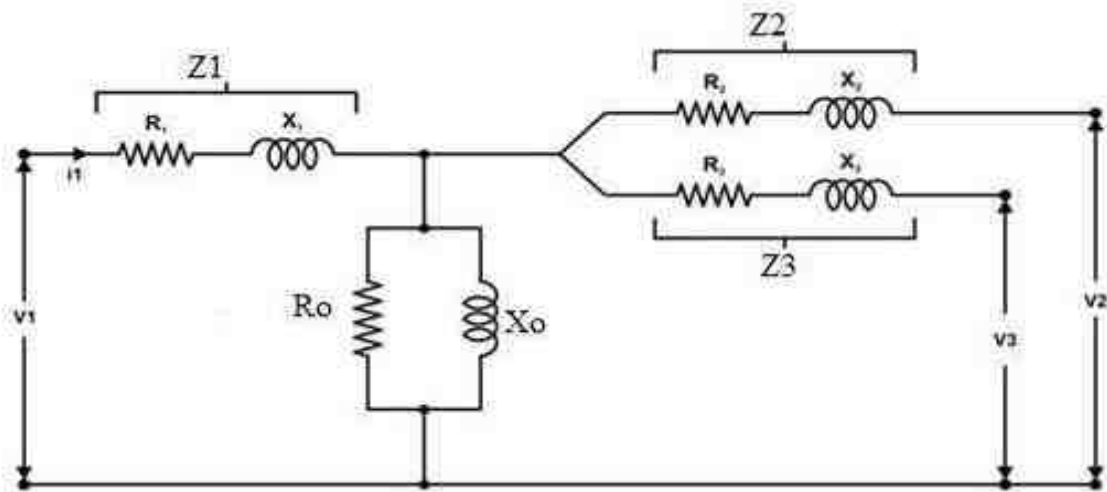From the above values draw the Equivalent circuit, as below




Result:

**Y-BUS FORMATION USING MATLAB**

**Problem :** Write a MATLAB program to develop the bus admittance matrix

**Aim:** To Write a MATLAB program to develop the bus admittance matrix for a given network.

**CIRCUIT DIAGRAM:**

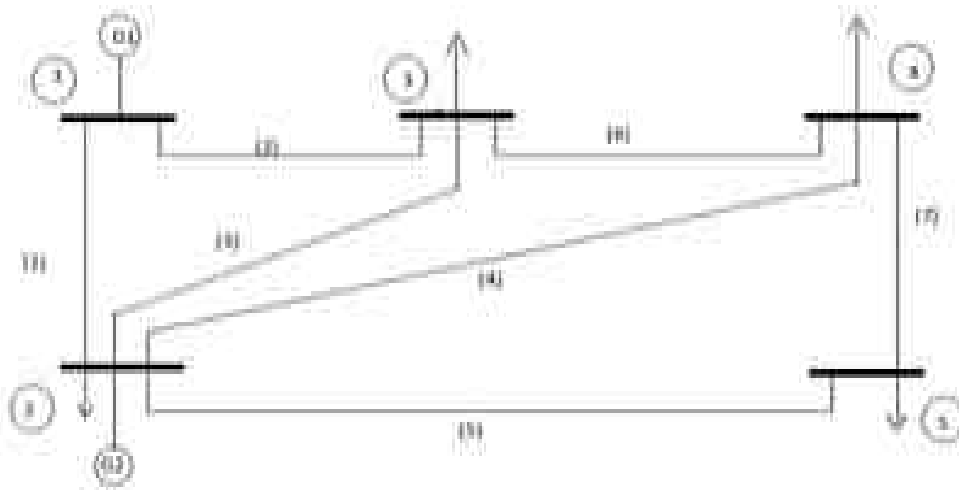

**Fig. Machine 5 - Bus System**

**Table: Bus Classification**

Type of Bus	No. of Buses
Slack Bus	1
Generator Bus	1
Load Bus system	3

Table: Impedances and Line charging admittance for the IEEE 5-bus system

**MATLAB Program for YBUS with shunt capacitance of the power system**

```

%           Line code
%   Bus bus R   X   1/2 B = 1 for lines
%   nl nr p.u. p.u. p.u. > 1 or < 1 tr. tap at bus nl
linedata=[ 1   2   0.02  0.06  0.03
           1   3   0.08  0.24  0.025
           2   3   0.06  0.18  0.02
           2   4   0.06  0.18  0.02
           2   5   0.04  0.12  0.015
           3   4   0.01  0.03  0.01
           4   5   0.08  0.24  0.025 ];
j=sqrt(-1);
nl=linedata(:,1); nr=linedata(:,2);
    
```

```

R=linedata(:,3); X=linedata(:,4);
BC=j*linedata(:,5);
a=linedata(:,6);
nbr=length(linedata(:,1)); nbus=max(max(nl),max(nr));
Z=R+j*X;
Y=ones(nbr,1)./Z;
for n=1:nbr
    if a(n)<=0 a(n)=1;
    else end
    Ybus=zeros(nbus,nbus);
for k=1:nbr;
    Ybus(nl(k),nr(k))=Ybus(nl(k),nr(k))-Y(k)/a(k)
    Ybus(nr(k),nl(k))=Ybus(nl(k),nr(k))
end
end
for n=1:nbus
    for k=1:nbr
        if nl(k)==n
            Ybus(n,n)= Ybus(n,n)+Y(k)/(a(k)^2)+BC(k)
        else if nr(k)==n
            Ybus(n,n)=Ybus(n,n)+Y(k)+BC(k)
        else, end
    end
end
end

```

### Output:

```

Ybus=
[6.2500 -18.6950i -5.0000 +15.0000i -1.2500 + 3.7500i    0          0
-5.0000 +15.0000i 10.8333 -32.4150i -1.6667 + 5.0000i -1.6667 + 5.0000i -2.5000 + 7.5000i
-1.2500 + 3.7500i -1.6667 + 5.0000i 12.9167 -38.6950i -10.0000 +30.0000i    0
0          -1.6667 + 5.0000i -10.0000 +30.0000i 12.9167 -38.6950i -1.2500 + 3.7500i
0          -2.5000 + 7.5000i    0          -1.2500 + 3.7500i  3.7500 -11.2100i]

```

### Precautions:


1. Check and write the program without errors.
2. Properly turn on and turn off your pc

### Results:

**Z-BUS FORMATION USING MATLAB**

**Problem:** Write a MATLAB program to develop the bus impedance matrix

**Aim:** To Write a MATLAB program to develop the bus impedance matrix for a given network.

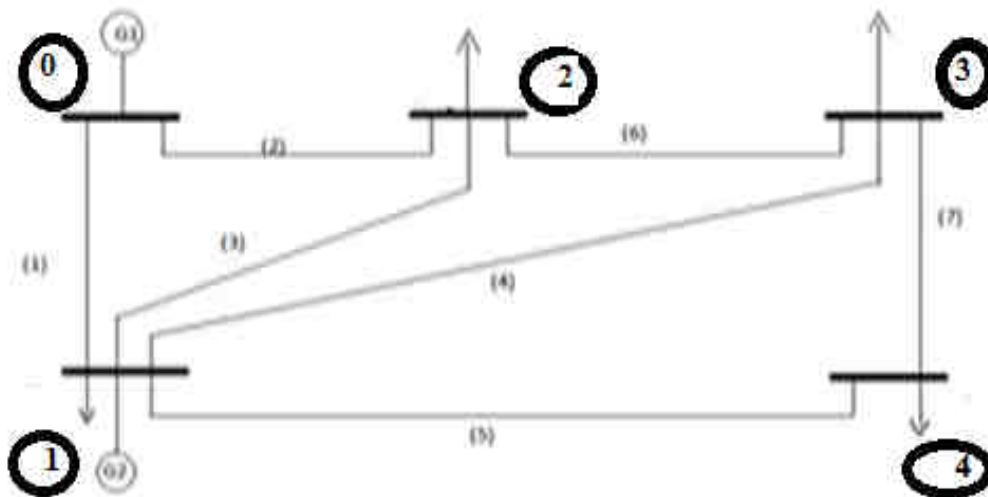

**Fig. -Machine 5-Bus System**

**Table: Bus Classification**

Type of Bus	No. of Buses
Slack Bus	1
Generator Bus	2
Load Bus system	3

Table: Impedances and Line charging admittance for the IEEE 5-bus syst

**MATLAB Program for the formation of  $Z_{bus}$  without shunt capacitance of the power system**

```

%*Formation of Zbus without shunt capacitance of the power system*%
linedata=[ 0  1 0.02  0.06
           0  2 0.08  0.24
           1  2 0.06  0.18
           1  3 0.06  0.18
           1  4 0.04  0.12
           2  3 0.01  0.03
           3  4 0.08  0.24];
% function [Zbus] = zbuild(linedata)
nl = linedata(:,1);
nr = linedata(:,2);
    
```

```

R = linedata(:,3);
X = linedata(:,4);
nbr=length(linedata(:,1)); nbus = max(max(nl), max(nr));
for k=1:nbr
if R(k) == inf | X(k) ==inf
    R(k) = 99999999; X(k) = 99999999;
else, end
end

ZB = R + j*X;
Zbus = zeros(nbus, nbus);
tree=0; %%%new
% Adding a branch from a new bus to reference bus 0
for I = 1:nbr
    ntree(I) = 1;
if nl(I) == 0 | nr(I) == 0
if nl(I) == 0    n = nr(I);
elseif nr(I) == 0 n = nl(I);
end
if abs(Zbus(n, n)) == 0  Zbus(n,n) = ZB(I);tree=tree+1; %%%new
else Zbus(n,n) = Zbus(n,n)*ZB(I)/(Zbus(n,n) + ZB(I));
end
        ntree(I) = 2;
else,end
end

% Adding a branch from new bus to an existing bus
while tree < nbus %%% new

for n = 1:nbus
    nadd = 1;
if abs(Zbus(n,n)) == 0
for I = 1:nbr
if nadd == 1;
if nl(I) == n | nr(I) == n
if nl(I) == n    k = nr(I);
elseif nr(I) == n k = nl(I);
end
if abs(Zbus(k,k)) ~= 0
for m = 1:nbus
if m ~= n
                Zbus(m,n) = Zbus(m,k);
                Zbus(n,m) = Zbus(m,k);

else, end
end
                Zbus(n,n) = Zbus(k,k) + ZB(I); tree=tree+1; %%%new
                nadd = 2; ntree(I) = 2;

else, end
else, end
else, end
end
else, end
end
end%%%%new

% Adding a link between two old buses
for n = 1:nbus
for I = 1:nbr
if ntree(I) == 1
if nl(I) == n | nr(I) == n
if nl(I) == n    k = nr(I);
elseif nr(I) == n k = nl(I);
end
        DM = Zbus(n,n) + Zbus(k,k) + ZB(I) - 2*Zbus(n,k);
for jj = 1:nbus

```

```

        AP = Zbus(jj,n) - Zbus(jj,k);
for kk = 1:nbus
    AT = Zbus(n,kk) - Zbus(k, kk);
    DELZ(jj,kk) = AP*AT/DM;
end
end

    Zbus = Zbus - DELZ;
    ntree(l) = 2;
else,end
else,end
end
end
    Zbus

```

**Output:**

**Zbus =**

```

[0.0169 + 0.0506i  0.0126 + 0.0377i  0.0134 + 0.0403i  0.0157 + 0.0471i
 0.0126 + 0.0377i  0.0297 + 0.0891i  0.0263 + 0.0789i  0.0171 + 0.0514i
 0.0134 + 0.0403i  0.0263 + 0.0789i  0.0317 + 0.0951i  0.0195 + 0.0586i
 0.0157 + 0.0471i  0.0171 + 0.0514i  0.0195 + 0.0586i  0.0437 + 0.1310i];

```

**Result:**



### Gauss-Seidel load flow analysis using MATLAB

**Problem:** for the IEEE-5 bus system shown in figure, obtain the complete load flow solution using Gauss-seidal load flow analysis method using MATLAB.

**Aim:** To develop a computer program to solve the set of non linear load flow equations using Gauss seidal load flow algorithm.

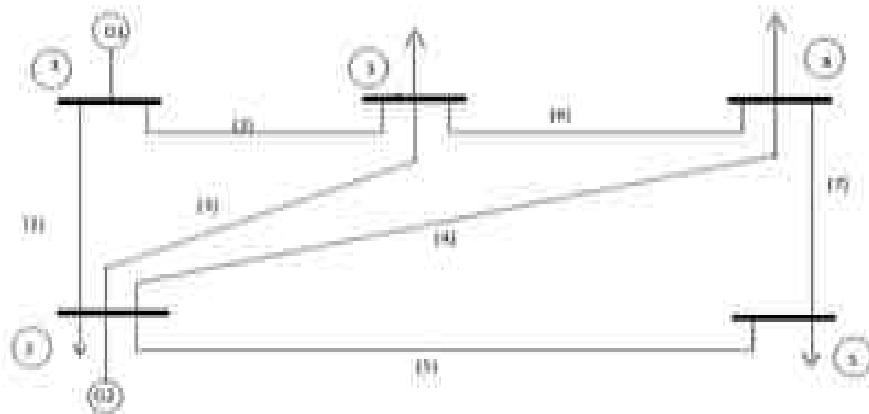


Fig. Machine 5 - Bus System

Table: Bus Classification

Type of Bus	No. of Buses
Slack Bus	1
Generator Bus	1
Load Bus system	3

Table: Impedances and Line charging admittance for the IEEE 5-bus system

Bus Code p-q	Impedance $Z_{pq}$	Line Charging $Y_{pq}/2$	Off nominal Tap setting

## Program

```

clc
basemva=100; accuracy=0.001; accel=1.4;
maxiter=100;
%           Line code
%   Bus bus R   X   1/2 B   = 1 for lines
%   nl nr p.u. p.u. p.u.   > 1 or < 1 tr. tap at bus nl
linedata=[ 1 2 0.02 0.06 0.03 1
           1 3 0.08 0.24 0.025 1
           2 3 0.06 0.18 0.02 1
           2 4 0.06 0.18 0.02 1
           2 5 0.04 0.12 0.015 1
           3 4 0.01 0.03 0.01 1
           4 5 0.08 0.24 0.025 1];
%IEEE5-BUS TEST SYSTEM
%bus bus voltage angle load generator static mvar
%no code mag degree mw mvar mw mvar qmin qmax +qc/-q1
busdata=[1 1 1.06 0 0 0 0 0 0 0 0
          2 2 1.0 0 20 10 40 30 0 0 0
          3 0 1.0 0 45 15 0 0 0 0 0
          4 0 1.0 0 40 5 0 0 0 0 0
          5 0 1.0 0 60 10 0 0 0 0 0];
lfybus
lfgauss
busout
lineflow

```

## Output:

### Ybus=

```

[6.2500 -18.6950i    -5.0000 +15.0000i    -1.2500 + 3.7500i         0         0
 -5.0000 +15.0000i    10.8333 -32.4150i    -1.6667 + 5.0000i    -1.6667 + 5.0000i    -2.5000 +
 7.5000i
 -1.2500 + 3.7500i    -1.6667 + 5.0000i    12.9167 -38.6950i    -10.0000 +30.0000i         0
 0                    -1.6667 + 5.0000i    -10.0000 +30.0000i    12.9167 -38.6950i    -1.2500 +
 3.7500i
 0                    -2.5000 + 7.5000i         0                    -1.2500 + 3.7500i    3.7500 -
 11.2100i]

```

### Power Flow Solution by Gauss-Seidel Method

Maximum Power Mismatch = 0.000406446

No. of Iterations = 11

Bus Voltage Angle -----Load----- ---Generation--- Injected

No.	Mag.	Degree	MW	Mvar	MW	Mvar	Mvar
1	1.060	0.000	0.000	0.000	131.091	90.823	0.000
2	1.000	-2.061	20.000	10.000	40.000	-61.605	0.000

3	0.987	-4.636	45.000	15.000	0.000	0.000	0.000
4	0.984	-4.957	40.000	5.000	0.000	0.000	0.000
5	0.972	-5.765	60.000	10.000	0.000	0.000	0.000

**Total            165.000   40.000   171.091   29.218   0.000**

Line Flow and Losses

	--Line-- Power at bus & line flow			--Line loss--		Transformer		
	from	to	MW	Mvar	MVA	MW	Mvar	tap
1	131.091	90.823	159.479					
2	89.323	73.998	115.992	2.486	1.086			
3	41.788	16.821	45.046	1.518	-0.693			
2	20.000	-71.605	74.346					
1	-86.837	-72.912	113.388	2.486	1.086			
3	24.471	-2.518	24.601	0.359	-2.871			
4	27.713	-1.724	27.767	0.461	-2.554			
5	54.660	5.558	54.942	1.215	0.729			
3	-45.000	-15.000	47.434					
1	-40.270	-17.514	43.913	1.518	-0.693			
2	-24.112	-0.352	24.114	0.359	-2.871			
4	19.396	2.862	19.606	0.040	-1.823			
4	-40.000	-5.000	40.311					
2	-27.253	-0.830	27.265	0.461	-2.554			
3	-19.356	-4.685	19.915	0.040	-1.823			
5	6.598	0.519	6.619	0.043	-4.652			
5	-60.000	-10.000	60.828					
2	-53.445	-4.829	53.663	1.215	0.729			
4	-6.555	-5.171	8.349	0.043	-4.652			
<b>Total loss</b>			<b>6.122</b>	<b>-10.778</b>				

**Result:**

NEWTON RAPHSON LOAD FLOW ANALYSIS USING SOFT TOOLS

**Problem:** for the IEEE-5 bus system shown in figure, obtain the complete load flow solution using Newton Raphson load flow analysis method using MATLAB.

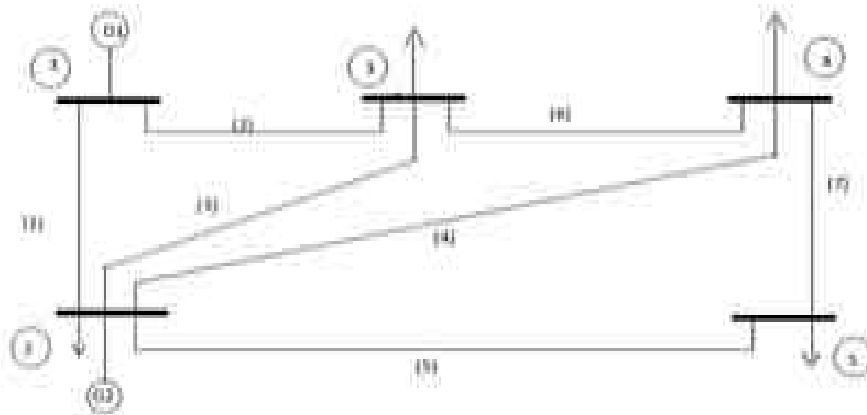


Fig-9.1 Machine 5 - Bus System

Table: Bus Classification

Type of Bus	No. of Buses
Slack Bus	1
Generator Bus	1
Load Bus system	3

Table: Impedances and Line charging admittance for the IEEE 5-bus system

Bus Code p-q	Impedance $Z_{pq}$	Line Charging $Y_{pq}/2$	Off nominal Tap setting

**Table:** Scheduled generation and loads and assumed bus voltages for IEEE 5-bus system

Bus No	Assumed bus voltage	Generation		Load	
		MW	Mvar	MW	Mvar

**Aim:** To develop a computer program to solve the set of non linear load flow equations using Newton Rhapshon load flow Method.

**Program**

```

clear
basemva=100; accuracy=0.001; accel=1.4;
maxiter=100;
%                               Line code
%   Bus bus  R    X   1/2 B  = 1 for lines
%   nl nr p.u. p.u. p.u.  > 1 or < 1 tr. tap at bus nl
linedata=[ 1 2 0.02 0.06 0.03 1
           1 3 0.08 0.24 0.025 1
           2 3 0.06 0.18 0.02 1
           2 4 0.06 0.18 0.02 1
           2 5 0.04 0.12 0.015 1
           3 4 0.01 0.03 0.01 1
           4 5 0.08 0.24 0.025 1];
%IEEE5-BUS TEST SYSTEM
%bus bus voltage angle load generator static mvar
%no code mag degree mw mvar mw mvar qmin qmax +qc/-q1
busdata=[1 1 1.06          0 0 0 0 0 0 0
         2 2 1.0   0 20 10 40 30 0 0 0
         3 0 1.0   0 45 15 0 0 0 0 0
         4 0 1.0   0 40 5 0 0 0 0
         0 1.0 0   60 10 0 0 0 0 0];
lfybus
lfnewton
busout
lineflow
    
```

**Result:**

**Ybus=**

[6.2500 -18.6950i	-5.0000 +15.0000i	-1.2500 + 3.7500i	0	0
-5.0000 +15.0000i	10.8333 -32.4150i	-1.6667 + 5.0000i	-1.6667 + 5.0000i	-2.5000 +
7.5000i				
-1.2500 + 3.7500i	-1.6667 + 5.0000i	12.9167 -38.6950i	-10.0000 +30.0000i	0
0	-1.6667 + 5.0000i	-10.0000 +30.0000i	12.9167 -38.6950i	-1.2500 +
3.7500i				
0	-2.5000 + 7.5000i	0	-1.2500 + 3.7500i	3.7500 -
11.2100i ]				

**Power Flow Solution by Newton-Raphson Method**

**Maximum Power Mismatch = 7.81261e-005**

**No. of Iterations = 3**

**Bus Voltage Angle -----Load----- ---Generation--- Injected**  
**No. Mag. Degree MW Mvar MW Mvar Mvar**

1	1.060	0.000	0.000	0.000	131.114	90.815	0.000
2	1.000	-2.061	20.000	10.000	40.000	-61.607	0.000
3	0.987	-4.637	45.000	15.000	0.000	0.000	0.000
4	0.984	-4.957	40.000	5.000	0.000	0.000	0.000
5	0.972	-5.765	60.000	10.000	0.000	0.000	0.000
<b>Total</b>			<b>165.000</b>	<b>40.000</b>	<b>171.114</b>	<b>29.208</b>	<b>0.000</b>

**Line Flow and Losses**

**--Line-- Power at bus & line flow --Line loss-- Transformer**  
**from to MW Mvar MVA MW Mvar tap**

1	131.114	90.815	159.494			
2	89.331	73.995	115.997	2.486	1.087	
3	41.791	16.820	45.049	1.518	-0.692	
2	20.000	-71.607	74.348			
1	-86.846	-72.908	113.392	2.486	1.087	
3	24.473	-2.518	24.602	0.360	-2.871	
4	27.713	-1.724	27.767	0.461	-2.554	
5	54.660	5.558	54.942	1.215	0.729	
3	-45.000	-15.000	47.434			
1	-40.273	-17.513	43.916	1.518	-0.692	
2	-24.113	-0.352	24.116	0.360	-2.871	
4	19.386	2.865	19.597	0.040	-1.823	
4	-40.000	-5.000	40.311			
2	-27.252	-0.831	27.265	0.461	-2.554	
3	-19.346	-4.688	19.906	0.040	-1.823	
5	6.598	0.518	6.619	0.043	-4.652	
5	-60.000	-10.000	60.828			
2	-53.445	-4.829	53.663	1.215	0.729	
4	-6.555	-5.171	8.349	0.043	-4.652	

**Total loss                      6.122      -10.777**

**DEVELOP A MODEL FOR A UNCONTROLLED SINGLE AREA LOAD FREQUENCY CONTROL PROBLEM AND SIMULATE THE SAME USING SOFT TOOLS.**

**SIMULINK model for a single area load frequency problem**

**Problem:** Develop a SIMULINK model for single area power system to investigate the load frequency dynamics for a step load disturbance in the area. The parameters of the single area power system are as follows.

$$T_g=0.3\text{sec}, K_g=20$$

$$T_t= 0.5\text{sec}, K_t=.2$$


$$K_{ps}=100, T_{ps}=25\text{sec}, R=3$$

**Aim:** To develop a SIMULINK model for a single area power system to study the load frequency dynamics.

**Load Frequency Control:** Frequency regulation is the method to control the system frequency by maintaining a continuous balance between the generation and load demand within a control area. Whenever the power system is subjected to disturbances i.e. change in generation or load, the mismatch between the load and generation causes the system frequency to change. The off-nominal frequency can directly impact on power system operation and system reliability.


**AGC Controller:** The function of the controller is to generate, raise or lower the command signals to the speed gear changer of the prime mover in response to the area control error (ACE) signal by performing mathematical manipulations of amplification and integration of this signal and manipulated the generation to minimize the mismatch between load demand and generation.

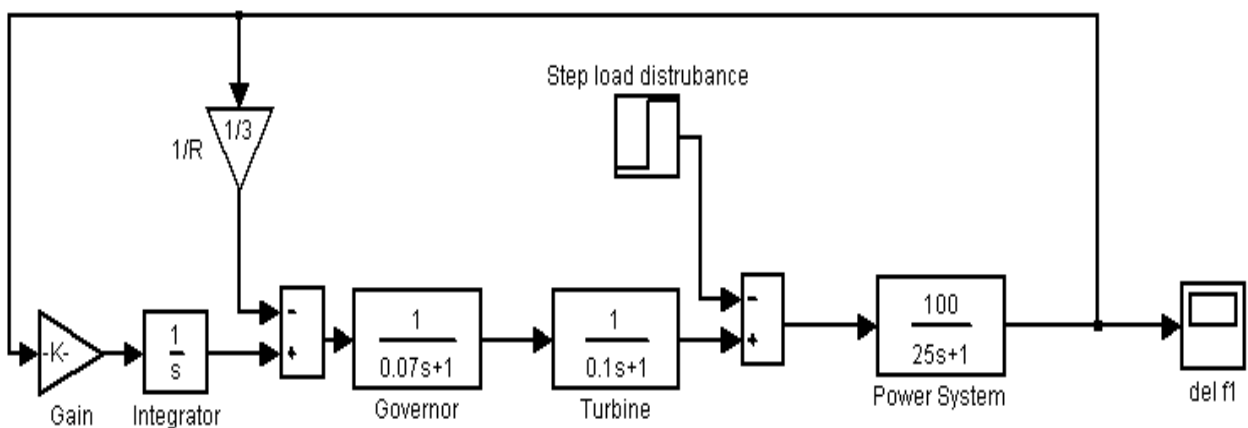**SIMULINK Block diagram representation of single area power system.**




## Output
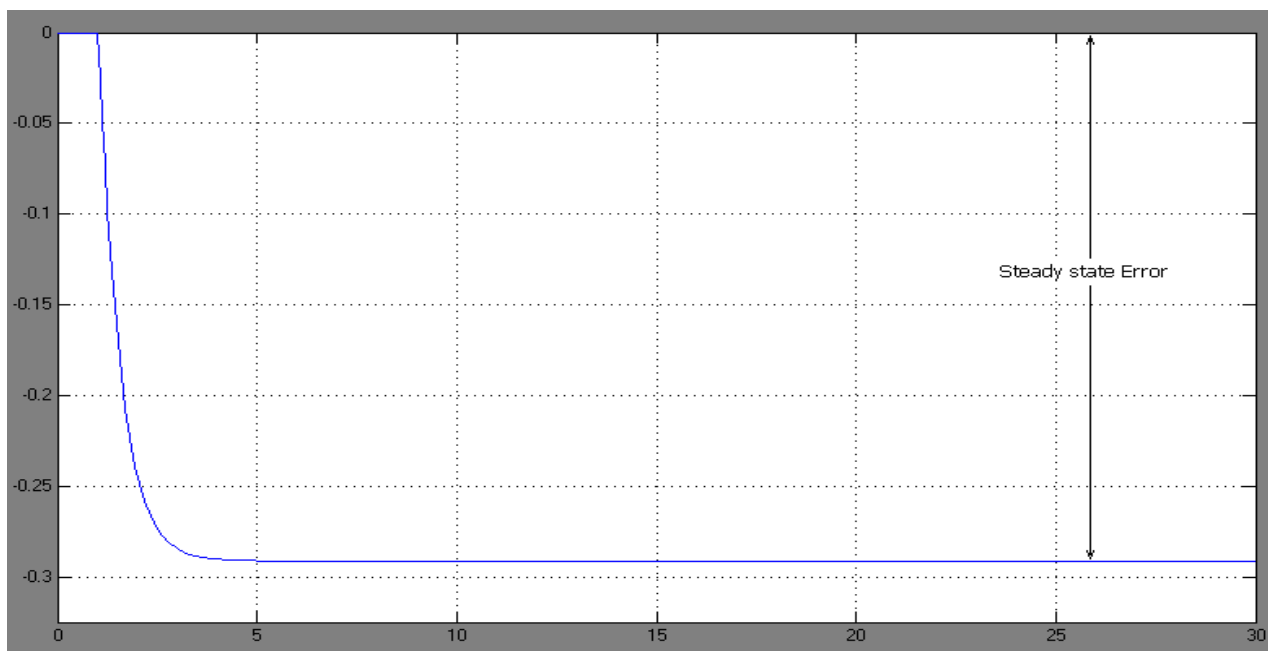
### Change in frequency without integral controller


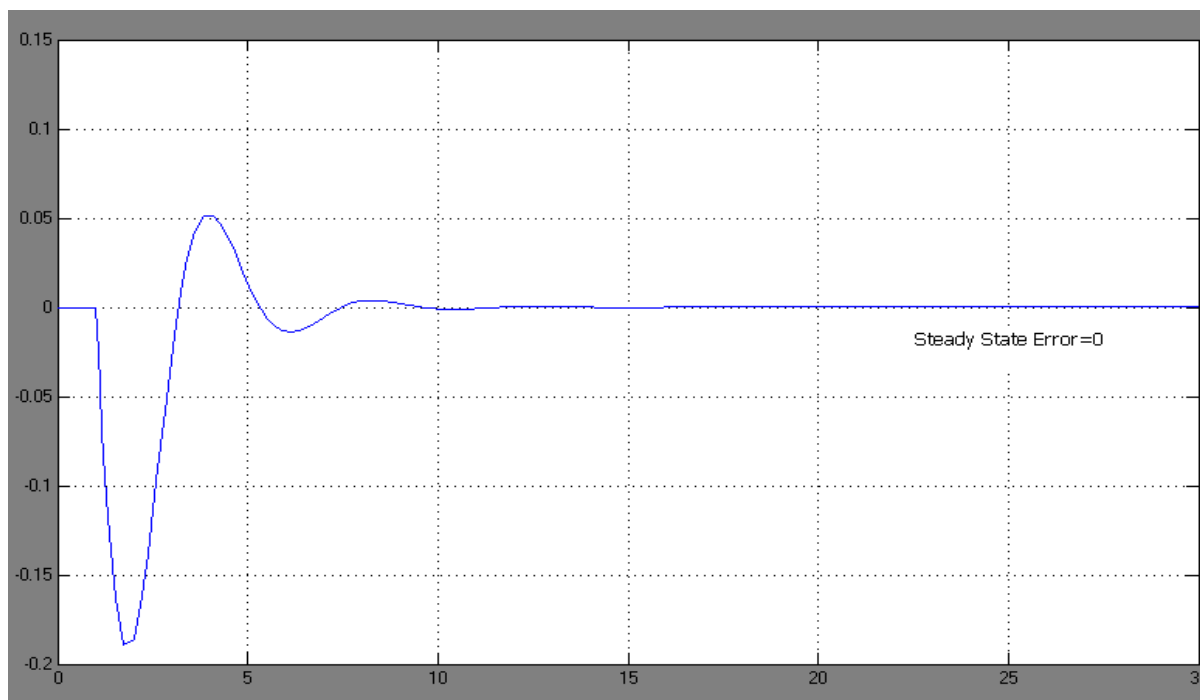
### Change in frequency with integral controller



**Result:** The load frequency dynamics in a single area power system has been investigated and the influence of integral controller on the LFC dynamics was investigated.



**DEVELOP A MODEL FOR A UNCONTROLLED TWO AREA LOAD FREQUENCY CONTROL PROBLEM AND SIMULATE THE SAME USING SOFT TOOLS.**

**SIMULINK model for a two area load frequency problem**

**Problem:** Obtain the MATLAB/SIMULINK model representation for 0.01stepload disturbance of two area power system to plot frequency and tie-line power dynamics in the controlled and uncontrolled case, use the following data.


$$T_{g1}=T_{g2}=0.45\text{sec}, K_{g1}=K_{g2}=1$$

$$T_{t1}= T_{t2}=0.55\text{sec}, K_{t1}=K_{t2}=1$$

$$K_{p1}=120, K_{p2}=80, T_{p1}=10\text{sec}, T_{p2}=20\text{sec}, R_1=2.5, R_2=3.625, T_{12}=0.4$$


**Aim:** To develop a SIMULINK model for a two area power system to study the load frequency dynamics.

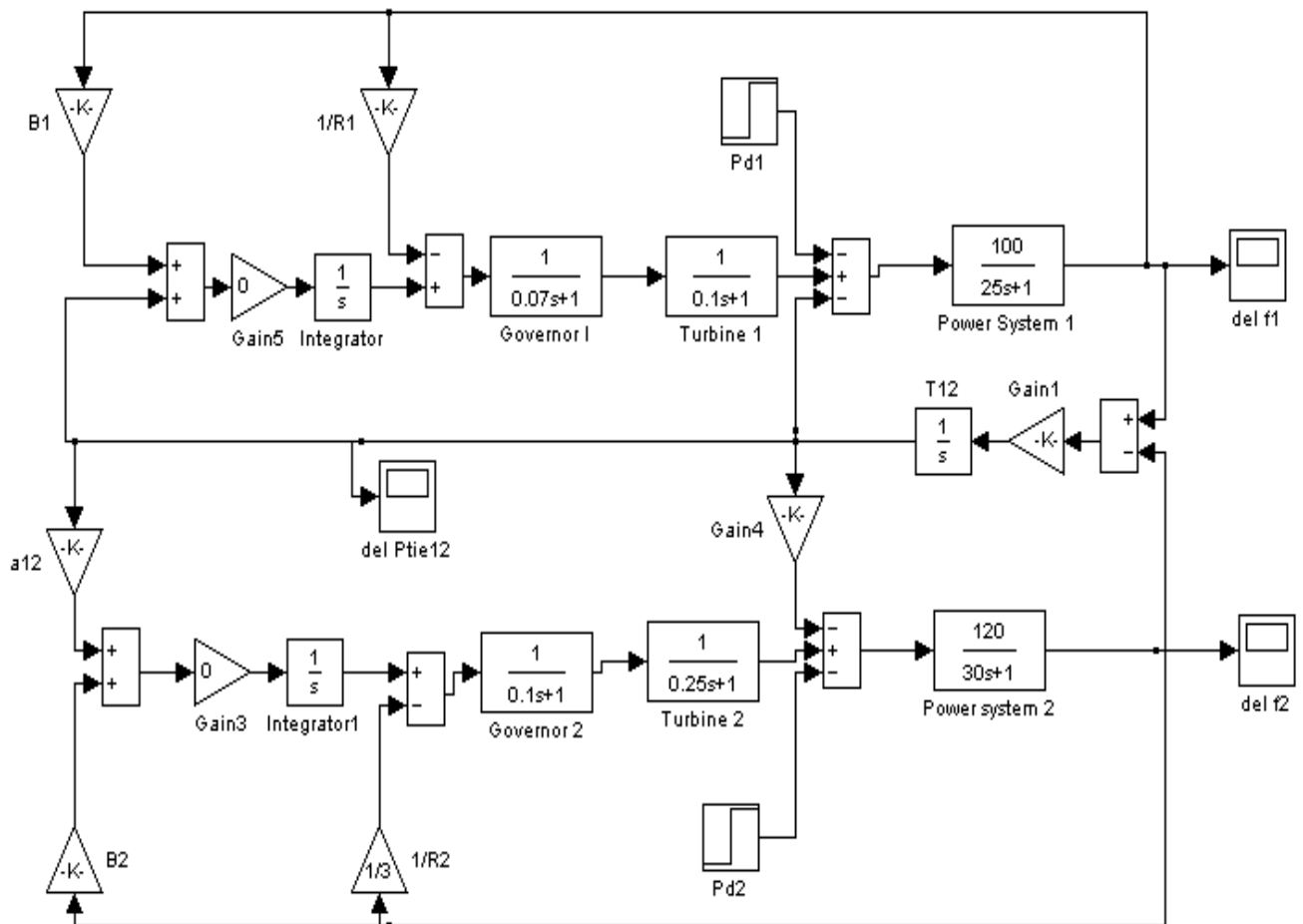**Block diagram of two area power system**




**Output:**


Change in frequency in area 1

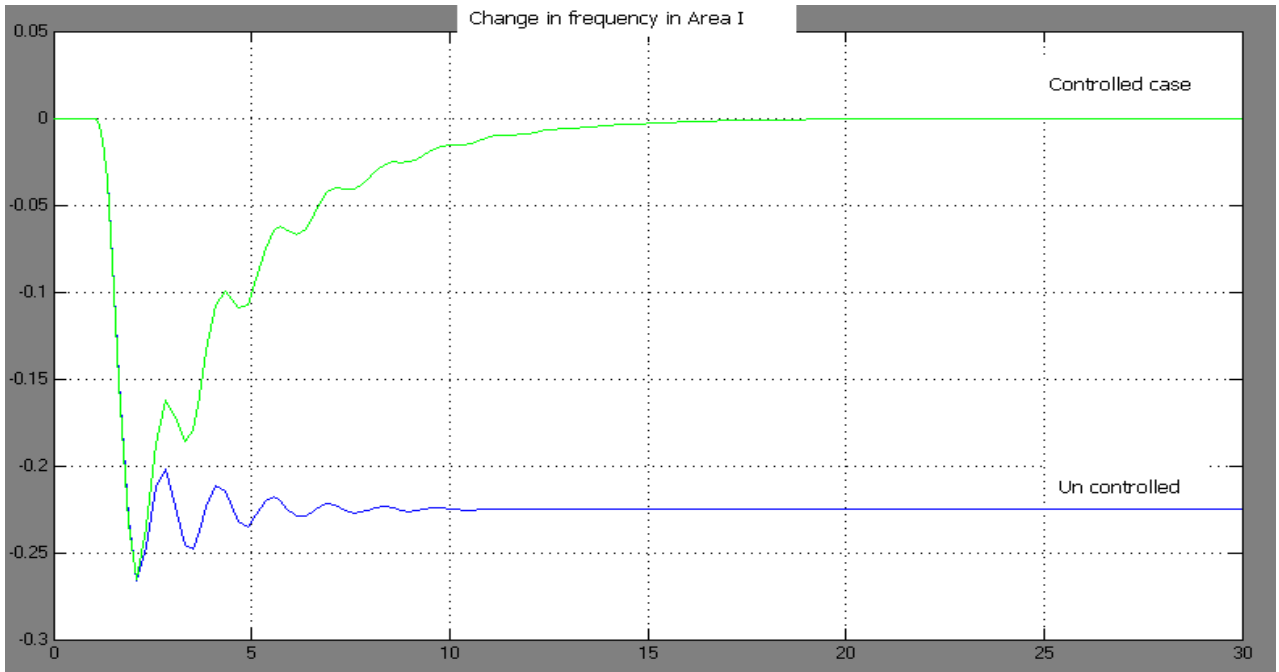

Change in frequency in area 2

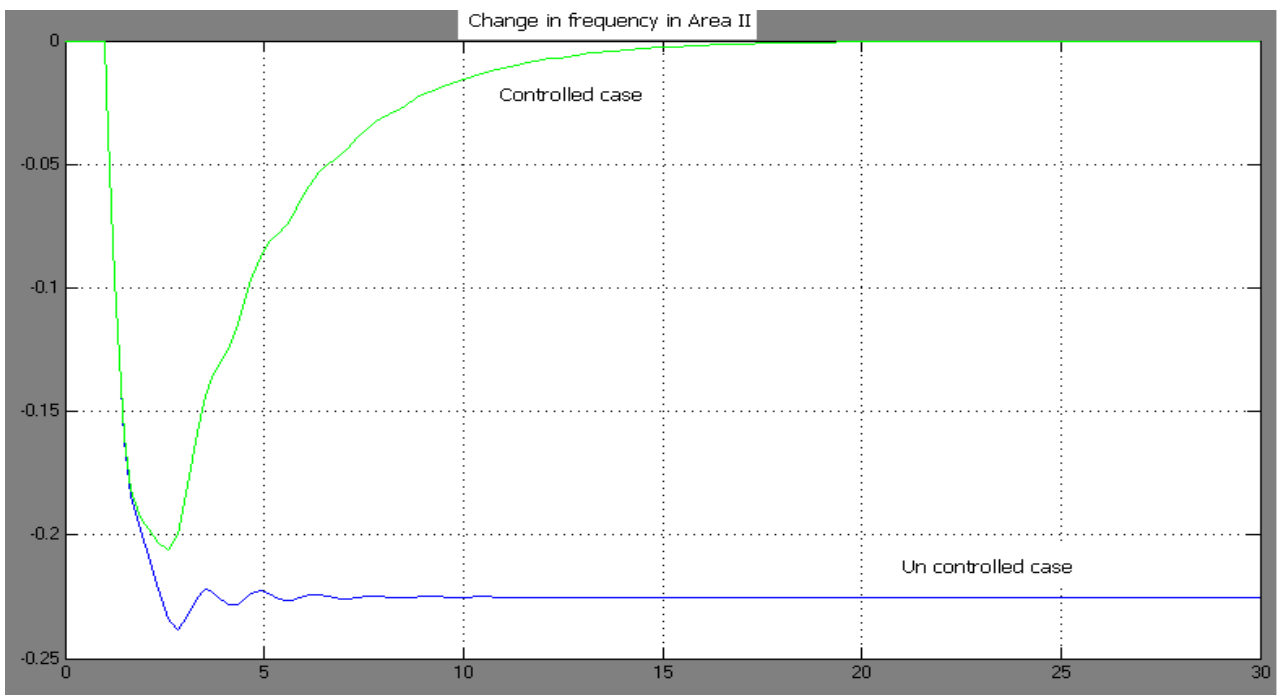

## Change in Tie-line power

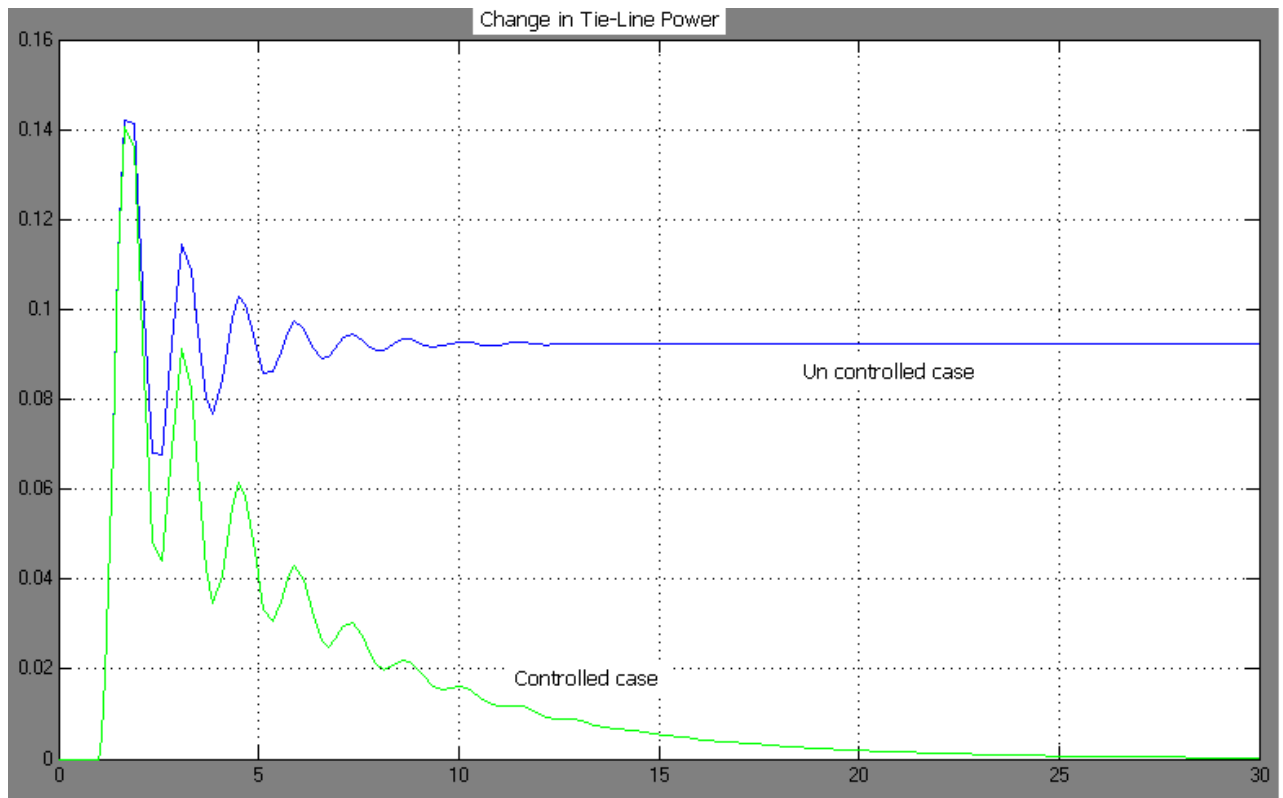

**Result:** The load frequency dynamics in a two area power system has been investigated and the influence of integral controller on the LFC dynamics was investigated.


**DEVELOP A PROGRAM TO SOLVE SWING EQUATION BY POINT BY POINT METHOD USING MATLAB**

**Problem:** Investigate the stability of the power system given using swing equation solved by Point-by-Point method.

**System data:**  $f = 50\text{hz}$  generator 50 MVA supplying 50 MW with inertia constant 'H' = 2.7 MJ/MVA at rated speed.  $E = 1.05\text{ pu}$ ,  $V = 1\text{ pu}$ ,  $X_1 = X_2 = 0.4\text{ pu}$ . three phase fault at line 2.

- (a) plot swing curve for a sustained fault up to a time of 5 secs.
- (b) Plot swing curve if fault is cleared by isolating line in 0.1 seconds.
- (c) Find the critical clearing angle


One line diagram

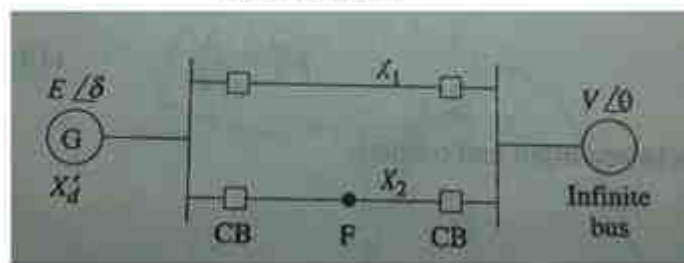

**Aim:** To solve the swing equation using Point-by-point method and apply it to investigate the stability of the power system.

The line diagram of the system during the fault is shown in the figure.

Impedance diagram during fault

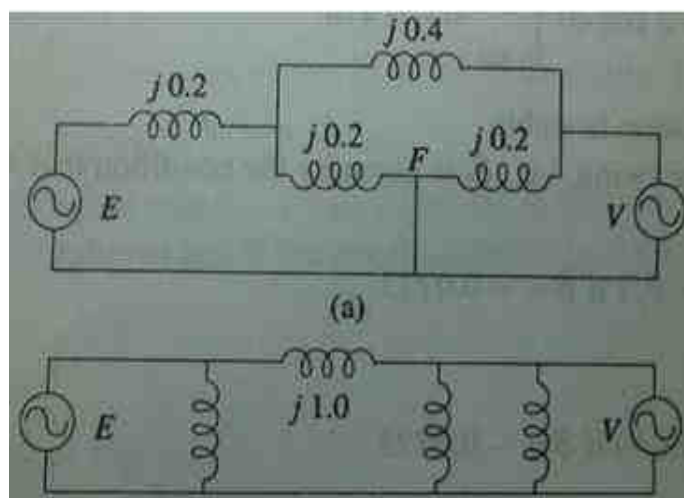

## Program:

```
clc;
close all

E = 50; V = 1; Xd = 0.2; X1 = 0.4; X2 = 0.4; H = 2.7;

% pre-fault condition

del = 0:pi/10:pi;
del1 = del;
del2 = del;

M = 2.7/(180*50); % angular momentum = H/180*f
Peo = (1.05/0.4)*sin(del); % Initial power curve
Po = 1; % power output in pu = 50 MW/50 MVA
delo = asind(0.4/1.05); % initial load angle in degrees //Pe =
(E*V/X) sin(delo)
% During fault

Pe2 = 1.05*sin(del1); % Power curve during fault

% Post fault condition

Pe3 = (1.05/0.6)*sin(del2); % Power curve after clearing fault

%% Primary Power curve plot Figure-1

plot(del, Peo);
set(gca, 'XTick', 0:pi/10:pi);
set(gca, 'XTickLabel', {'0', '', '', '', '', 'pi/2', '', '', '', 'pi'});
title('Power Curve');
xlabel('Load angle');
ylabel('Genpower');
text((2/3)*pi, (1.05/0.4)*sin((2/3)*pi), '\leftarrow initial
curve', 'HorizontalAlignment', 'left');
text(pi/2, 2.75, '2.625*sin\delta', 'HorizontalAlignment', 'center');
holdall
plot(del1, Pe2);
text((2/3)*pi, 1.05*sin((2/3)*pi), '\leftarrow during
fault', 'HorizontalAlignment', 'left');
text(pi/2, 1.80, '1.05*sin\delta', 'HorizontalAlignment', 'center');
plot(del2, Pe3);
text((2/3)*pi, (1.05/0.6)*sin((2/3)*pi), '\leftarrow fault
cleared', 'HorizontalAlignment', 'left');
text(pi/2, 1.1, '1.75*sin\delta', 'HorizontalAlignment', 'center');
holdoff

t = 0.05; % time step preferably 0.05 seconds
t1 = 0:t:0.5;

%% (a) sustained fault at t = 0

% for discontinuity at t = 0, we take the average of accelerating power
% before and after the fault
% at t = 0-, Pa1 = 0
% at t = 0+, Pa2 = Pi - Pe2
% at t = 0, Pa = Pa1 + Pa2/2

Pao = (1 - (1.05*sind(delo)))/2; % at the instant of fault del1 = delo
Pa(1) = Pao;
cdel(1) = 0;
d1 = t^2/M;
```

```

fori = 1:11

ifi == 1

d2(i) = d1*Pa(i);
del(i) = delo;

else
cdel(i) = cdel(i-1)+d2(i-1);

del(i) = del(i-1)+cdel(i);

Pe(i) = 1.05*sind(del(i));

Pa(i) = 1 - Pe(i);

d2(i) = d1*Pa(i);
end
end
%% swing curve 1 plot

figure (2);
plot(t1,del);
set(gca,'Xtick',0:0.05:0.5);
set(gca,'XtickLabel',{'0','0.05','0.10','0.15','0.20','0.25','0.30','0.35',
'0.40','0.45','0.50'});
title('Swing Curve');
xlabel('seconds');
ylabel('degrees');
text(0.30,150,' Sustained fault','HorizontalAlignment','right');
text(0.001,130,' load angle increases with time -- Unstable
state','HorizontalAlignment','left');
%% (b) Fault cleared in 0.10 seconds ,2nd step ---- 3rd element [1]0
[2]0.05,[3]0.10
Pafo = (1 - (1.05*sind(delo)))/2; % at the instant of fault dell =
delo
Paf(1) = Pao;
cdelf(1) = 0;
d1f = t^2/M;

fori = 1:2

ifi == 1

d2f(i) = d1*Pa(i);
delf(i) = delo;

else
cdelf(i) = cdelf(i-1)+d2f(i-1);
delf(i) = delf(i-1)+cdelf(i);
Pef(i) = 1.05*sind(delf(i));
Paf(i) = 1 - Pef(i);
d2f(i) = d1*Paf(i);
end

end
% after clearing fault, power curve shift to Pe3
fori = 3:11
ifi == 3

cdelf(i) = cdelf(i-1)+d2f(i-1);
delf(i) = delf(i-1)+cdelf(i);
Pef(i) = 1.05*sind(delf(i));
Paf(i) = 1 - Pef(i);
a1 = Paf(i);
d2f(i) = d1*Paf(i);

```

```

        a2 = d2f(i);
Pef(i) = 1.75*sind(delf(i));
Paf(i) = 1 - Pef(i);
d2f(i) = d1*Paf(i);
Paf(i) = (Paf(i)+ a1)/2;
d2f(i) = (d2f(i) + a2)/2;

else




cdelf(i) = cdelf(i-1)+d2f(i-1);
delf(i) = delf(i-1)+cdelf(i);
Pef(i) = 1.75*sind(delf(i));
Paf(i) = 1 - Pef(i);
d2f(i) = d1*Paf(i);
end
end

figure (3);
plot(t1,delf);
set(gca, 'Xtick',0:0.05:0.5);
set(gca, 'XtickLabel', {'0', '0.05', '0.10', '0.15', '0.20', '0.25', '0.30', '0.35',
'0.40', '0.45', '0.50'});
title('Swing Curve');
xlabel('seconds');
ylabel('degrees');
text(0.25,57, ' Fault Cleared in 0.10 sec', 'HorizontalAlignment', 'right');
text(0.15,30, ' load angle decreases with time -- Stable
state', 'HorizontalAlignment', 'left');
%% (c) critical clearing angle
delo = delo*(pi/180); % initial load angle in rad
delm = pi - asin(1/1.75); % angle of max swing

c1 = ((delm-del0)-(1.05*cos(del0))+(1.75*cos(delm)))/(1.75-1.05);
cclang = acos(c1); % critical clearing angle
in rad
cclang = (180/pi)*(cclang); % critical clearing angle in
degree
cclang = int16(cclang); % converting to integer
fprintf('\n\n\t\t Critical Clearing angle is %d degree \n',cclang);

```

# Output

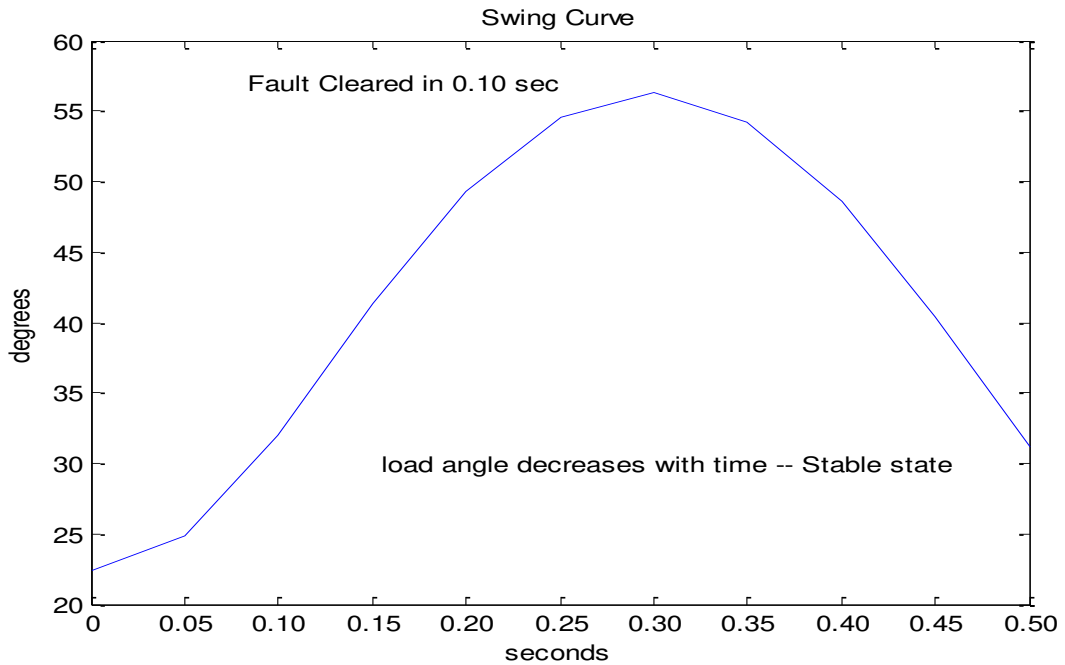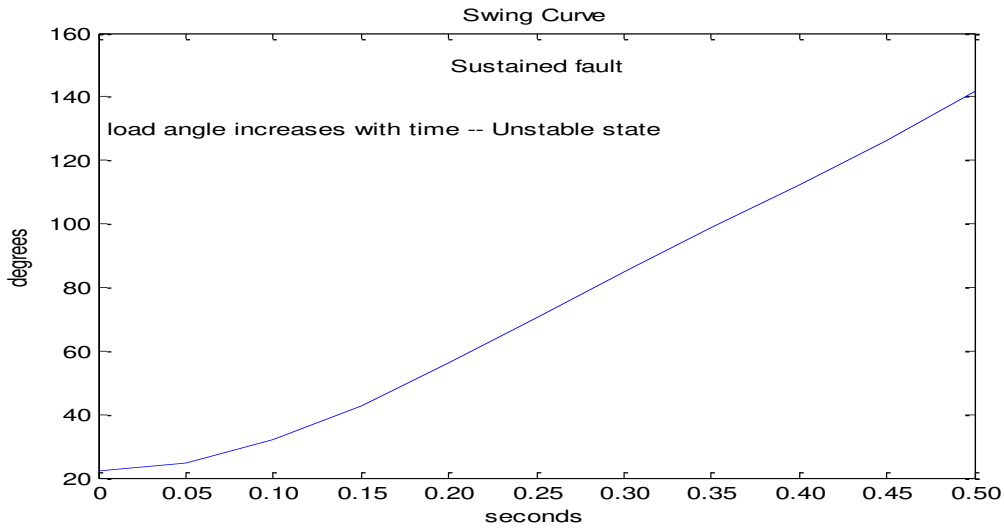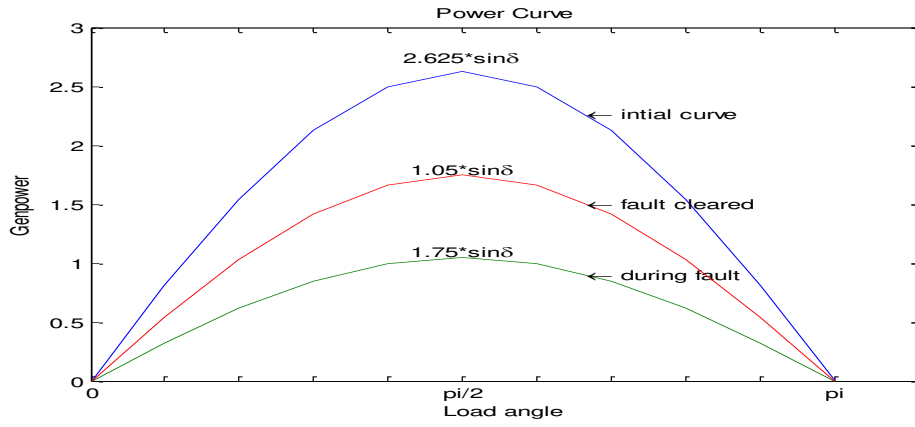

**Result:** The stability of the given system is investigated by using swing equation. The system is stable when the fault is cleared before the critical clearing time; the corresponding critical clearing angle for stability is  $112^\circ$ .